

Q-meter experiment

Shashvat Jain

Submitted to Dr. Daljeet Kaur
"32223904 - BASIC INSTRUMENTATION SKILLS"

Contents

1	Objective	1
2	Theory	1
3	Procedure	2
4	Result	2


1 Objective

Objective is to determine accurate **Quality Factor** of an unknown coil using the following arrangement.

2 Theory

The determination of the Quality factor Q using Q-meters is one of the most widely used means in the laboratory for testing radio frequency coils, inductors and capacitors.

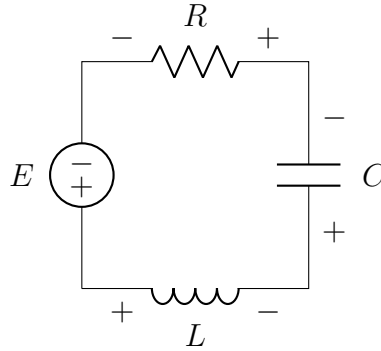The Quality factor is equal to $Q = \omega_0 L / R$ where ω_0 is the resonant frequency, L is the inductance and R is the effective resistance of the a coil. The effective resistance R , is never determined directly since its value depends upon the value of frequency.



Principle of Working

The principle of working of this useful laboratory instrument is based upon the well-known characteristics of a resonant series R-L-C circuit.

At resonant frequency f_0 , we have $X_C = X_L$ where capacitive reactance $X_C = \frac{1}{2\pi f_0 C}$, inductive reactance $X_L = 2\pi f_0 L$

and resonant frequency $f_0 = 1/(2\pi\sqrt{LC})$ and current at resonance $I_0 = E/R$ is then given by

The voltage across the capacitor $E_C = I_0 X_C = I_0 X_L = I_0 \omega_0 L$ and input voltage $E = I_0 * R$ then $E_C/E = (\omega_0 L)/R = Q$ and $E_C = QE$.

If the input voltage is kept constant the voltage across capacitor is Q times E and a voltmeter connected across the capacitor can be calibrated to read the value of Q directly.

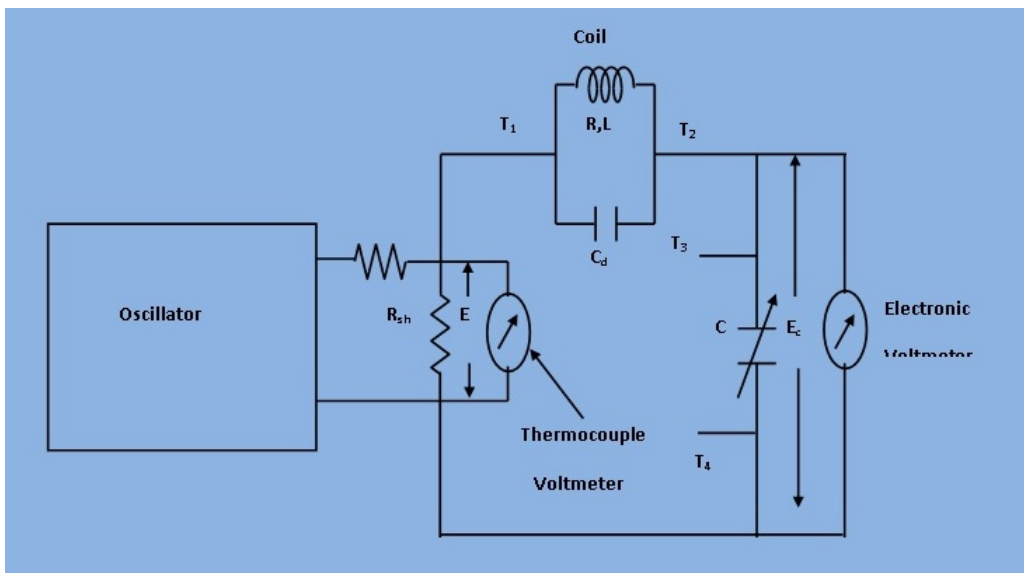


Figure 1: Circuit diagram for the arrangement of Q-meter

3 Procedure

1. Set the Shunt Resistance (R_{sh}) value as small as possible (Say 0.02 Ohm). Set all the parameters (R , L , C) by yourself.
2. Set the voltage value of the oscillator ($E=10$ V).
3. At $f=100$ Hz. Check the value of voltage drop across capacitor. (EC).
4. Change the frequency until EC reach at the maximum value. Then calculate the value Q measured using this formula $Q_{meas} = (\omega_0 L)/(R + R_{sh})$.
5. Calculate the true value of unknown coil by using this formula $Q_{true} = (\omega_0 L)/R$
6. First resonance occurs due to frequency (say f_1). Note down the value of tuning capacitor C . (say C_1). Double the input frequency (f_1) (say $f_2=2*f_1$). Change the tuning capacitor value until resonance occurs. Note down the value of tuning capacitor C . (say C_2). Discharge capacitance (C_d) would be $=(C_1-4*C_2)/3$.

4 Result

We obtain the following readings for $E = 10V, f_0 = 2700056$
 $V_c = 788.053581999041V, Q_{true} = 8.9507164206384$